

(Test provided by ETA International, http://www.eta-i.org/practice_exams/aststudy.htm)

Multiple Choice

Identify the choice that best completes the statement or answers the question.

1. What does the acronym ESD stand for?
 - a. Electrostatic Discharge
 - b. Electrostatic Device
 - c. Electromagnetic Sensitivity Diac
 - d. Electrostatic Damage

2. What is the number one concern in regards to electrical safety?
 - a. Proper grounding
 - b. ESD
 - c. Shock
 - d. Faulty equipment

3. Bohr's Atomic Model consists of what three components?
 - a. Neutrons, ion, neutrinos
 - b. Protons, neutrons and cations
 - c. Tachyons gravitons and electrons
 - d. Protons, neutrons and electrons

4. Electrons are arranged in _____ around a nucleus.
 - a. orthogonal lattices
 - b. shells
 - c. loops
 - d. spheres

5. What are three types of materials used in electronics?
 - a. Conductors, semi-conductors and insulators
 - b. Semi-conductors, insulators and semi-insulators
 - c. Insulators, conductors and interions
 - d. Conductors, insulators and regulators

6. Coulomb's Law describes the forces of attraction or repulsion between electrical charges, which are _____ to the product of the charges _____ to the distance between them.
 - a. directly proportional, inversely proportional
 - b. inversely proportional, directly proportional
 - c. indirectly proportional, directly proportional
 - d. inversely proportional, indirectly proportional

7. The magnetic field that surrounds a magnet can best be described as invisible lines of force, and are commonly referred to as:
- lines of flux.
 - lines of density.
 - lines of attraction.
 - lines of flux proportionality.
8. An analog multimeter (AMM) checks for:
- voltage, resistance and inductance.
 - voltage, resistance and capacitance.
 - current, resistance and capacitance.
 - voltage, current and resistance.
9. An oscilloscope with two vertical inputs, is commonly referred to as a _____ oscilloscope.
- multi-trace
 - dual-trace
 - sweep trigger-trace
 - modulation-trace
10. Voltage or potential difference is the measure of potential energy between two points in a circuit and is commonly referred to as:
- voltage drop.
 - voltage flow.
 - difference in conduction.
 - potential resistance.
11. What is impedance?
- The resistance of a component at a given frequency.
 - The conductivity of a component at a given frequency.
 - The potential difference of a component at a given frequency.
 - The ability of a component to store a charge at a given frequency.
12. A resistor has three color bands of red, brown and brown. What is the ohmic value of this resistor?
- 205 Ohms
 - 100 Ohms
 - 210 Ohms
 - 330 Ohms
13. What components value is measured in millihenries?
- Capacitor
 - Inductor
 - Resistor
 - Diode


14. Ohm's Law characterizes the relationship between:
- power, coulombs, current and joules.
 - inductance, resistance, current and joules.
 - power, resistance, current and voltage.
 - capacitance, inductance, voltage and current.
15. Ohm's Law states that resistance is calculated by voltage divided by current. Using Ohm's law, how do you determine power?
- Voltage times current
 - Current divided by resistance
 - Current squared, divided by resistance
 - Voltage divided by resistance
16. Using a scientific calculator, a 3300 ohm resistor can be entered with scientific notation as:
- 3.3×10^3
 - 33×10^3
 - 3.3×10^2
 - 330×10^2
17. Total resistance in a series circuit equals:
- half the measured resistance multiplied by the applied voltage.
 - the average value of the voltage drops across each resistor within the circuit.
 - The sum of the power dissipated by each resistor.
 - the sum of all the resistor values within the circuit.
18. If a series circuit has three resistors valued at 10k Ohms, 15k Ohms and 20k Ohms, with a voltage source of 15V, the total current will be_____.
- 333.33mA
 - 33.33uA
 - 333.33uA
 - 3.33uA
19. Current in a parallel circuit is:
- equally divided among each branch.
 - inversely proportional to the circuit's resistance.
 - equal to the sum of the branch resistances.
 - equal to the voltage source, minus the branch resistances.
20. With three 2.5k resistors and one 3.4k resistor in parallel, the total resistance is:
- 668.81k Ohms.
 - 66.29 Ohms.
 - 669.29 Ohms
 - 670.50k Ohms.

21. With one series 8 Ohm resistor connected to two in-parallel resistors, 20 and 30 ohms respectively, what is the total resistance (R_T)?
- 38 Ohms
 - 30 Ohms
 - 20 Ohms
 - 8 Ohms

22. Given a battery rated at 350 ampere-hours how many hours will the battery be able to provide 7 amperes?
- 25
 - 35
 - 50
 - 17.5


23. The basic properties associated with alternating voltage and current are:
- frequency, period, wavelength and amplitude.
 - frequency, deviation, wavelength and amplitude.
 - magnitude, period, wavelength and amplitude.
 - frequency, period, designation and amplitude.

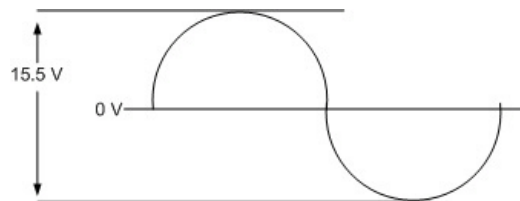24. What is the calculated effective voltage for the wave form below?




- 7.75V
- 5.48V
- 10.96V
- 4.933V

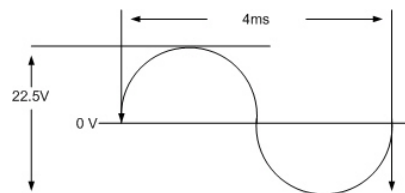25. What is the frequency of the sine wave below?



- 150Hz
- 250Hz
- 22.5KHz
- 150KHz

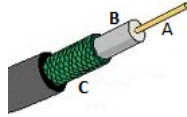26. In the illustration below, what component of the coaxial cable is letter "B"?




- a. Ground mesh
- b. Outer insulation
- c. Dielectric
- d. Center conductor

27. In an inductor/coil inductance varies as the _____ of the number of turns.

- a. Cube
- b. Square
- c. Inverse
- d. Log

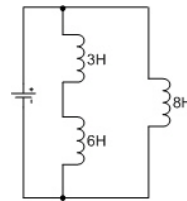28. What is the total inductance of the circuit below?



- a. 0.90H
- b. 4.24H
- c. 4.63H
- d. 9H

29. Two basic uses for transformers are:


- a. power supplies and bias control.
- b. signal matching and power supplies.
- c. signal matching and voltage regulation.
- d. voltage regulation and rectification.

30. What is meant by "transformer action"?


- a. The action in which an expanding and contracting magnetic field around the primary winding cuts the secondary winding and induces a direct voltage into the winding.
- b. The transfer of energy from one circuit to another circuit by magnetic rectification.
- c. The transfer of load voltage to the center-tapped secondary through capacitance.
- d. The transfer of energy from one circuit to another circuit by electromagnetic induction.

31. What are the three basic parts of a transformer?
- Primary winding, dielectric and core
 - Primary winding, secondary winding and core
 - Primary winding, power diode and secondary winding
 - Primary winding, secondary winding and tertiary winding

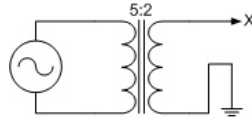32. In the circuit below, what is the voltage output at letter "X", when input voltage is 25V?




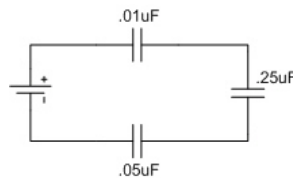- 25V
 - 5V
 - 15V
 - 10V
33. The time required to charge a capacitor to 63 percent is known as:
- Thevenin's constant.
 - a time constant.
 - a linear superposition.
 - Tau.
34. Given the series capacitive circuit below, what is the total capacitance?




- 0.008uF
 - 0.08uF
 - 0.076mF
 - 0.8uF
35. Calculate the capacitive reactance for 440 Hz and 9 uF.
- 44 Ohms
 - 0.02 Ohms
 - 37.37 Ohms
 - 40.21 Ohms
36. In a resistive-capacitive circuit the vector line relationship shows two lines perpendicular to each other. What is the phase relationship?
- In phase
 - Out of phase
 - 180 degree difference
 - 90 degree

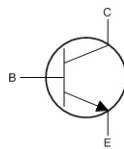37. In a capacitive circuit, what is the voltage and current relationship?
- Current lags
 - Voltage lags
 - Resistance leads
 - Voltage leads
38. When the frequency of an applied voltage is increased the capacitive reactance of a circuit will:
- decrease.
 - increase.
 - stay unchanged.
 - short all capacitors to ground.
39. What is the difference between calculating impedance for a series AC circuit and a parallel AC circuit?
- A series impedance calculation is derived from current and reactance, while parallel impedance is calculated with resistive and reactive current divided into the source current.
 - A series impedance calculation is derived from resistance and reactance, while parallel impedance is calculated with resistive and reactive current divided into the source voltage.
 - A series impedance calculation is derived from current and reactance, while parallel impedance is calculated with resistive and reactive current divided into the source voltage.
 - A series impedance calculation is derived from current and reactance, while parallel impedance is calculated with resistive and reactive voltage divided into the source current.
40. In a series resistive and reactive circuit what formula is used to find total impedance?
- $Z = X^2 \left(\frac{R^2}{2} \right)$
 - $Z = \sqrt{R^2 + X^2}$
 - $Z = R^2 \left(\frac{X^2}{2} \right)$
 - $Z = \sqrt{\frac{R^2 + X^2}{2}}$
41. Silicon diodes have an approximate voltage drop of:
- 0.3V
 - 0.7V
 - 1.414V
 - 0.9V
42. To properly bias the NPN transistor below, which voltages are correct?




- $E = +3; B = +1; C = -7$
- $E = -1; B = +1; C = +10$
- $E = -1.7; B = -2.7; C = -5$
- $E = 0; B = 0; C = +12$

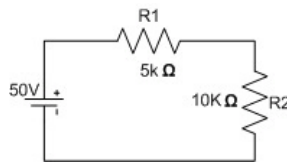43. Using ohm's law for the circuit below, calculate the total power.




- a. 166.6 mW
- b. 160.65 mW
- c. 16.6 mW
- d. 16 uW

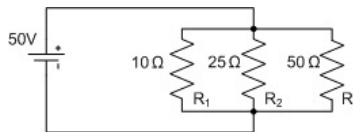44. In the circuit below, what is the current across R2?



- a. 5A
- b. 3.3A
- c. 2.5A
- d. 2A

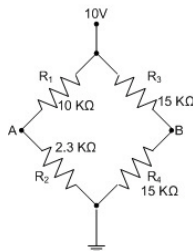45. What is the voltage at terminal 'A' for the Wheatstone bridge below?



- a. 10.3V
- b. 2.2V
- c. 1.3V
- d. 1.86V


46. What is a primary advantage of a FET when compared to the bipolar transistor?

- a. High input impedance
- b. Low input impedance
- c. Gate biasing is resistive controlled
- d. No advantage

47. Zener diodes are designed to operate in the _____ bias region.

- a. forward
- b. depletion
- c. reverse
- d. reactive

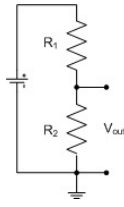48. What formula is used to properly calculate 'Vout' for the voltage divider below?



- a. $V_{out} = \left(\frac{R_2}{R_1+R_2}\right) V_{in}$
- b. $V_{out} = \left(\frac{R_1}{R_1+R_2}\right) V_{in}$
- c. $V_{out} = \left(\frac{R_1}{R_2+V_{in}}\right) V_{in}$
- d. $V_{out} = \left(\frac{R_2}{R_1R_2}\right) V_{in}$

49. When compared to a JFET, the base of a bipolar transistor is similar to what element of the JFET?

- a. Gate
- b. Drain
- c. Source
- d. Emitter

50. A MOSFET is comprised of what four elements?

- a. Gate, source, collector and substrate
- b. Gate, source, drain and substrate
- c. Base, source, drain and dielectric
- d. Dielectric, source, drain and base